

* CONCEPT OF FEEDBACK:-


Feedback is the process of taking some fraction from the output & feed back that portion to the input. This process is called feedback.

Types


(i) Positive feedback.

(ii) Negative feedback.


Positive
feed
back

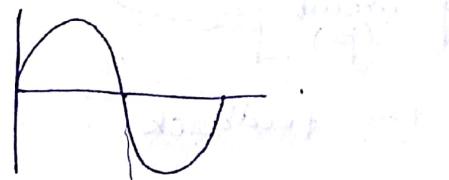

same phase

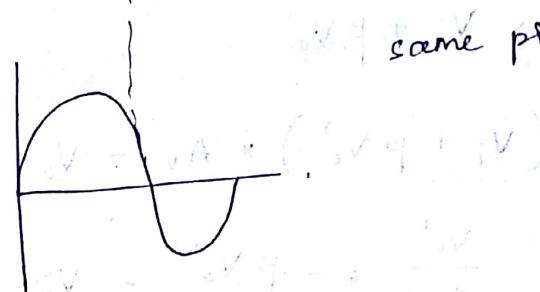

Negative
feedback.

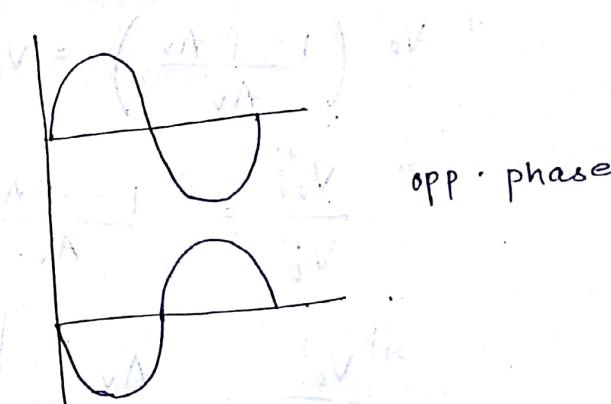


opp. phase

* PRINCIPLE OF FEEDBACK:-

$A_f \rightarrow$ gain of amplifier without feedback.

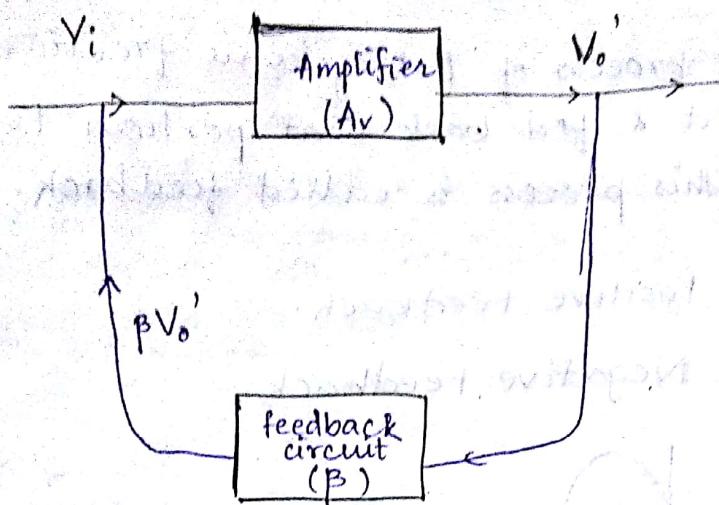$\beta \rightarrow$ feedback ~~factor~~ ratio.



Assuming the ne feedback,

$$\rightarrow V_i + \beta V_o'$$

$$\text{so, } (V_i + \beta V_o') \times A_v = V_o'$$

$$\therefore \frac{V_o'}{A_v} - \beta V_o' = V_i$$

$$\Rightarrow V_o' \left(\frac{1 - \beta A_v}{A_v} \right) = V_i$$

$$\text{ratio of } \frac{V_o'}{V_o} = \frac{1 - \beta A_v}{A_v}$$

$$\Rightarrow \frac{V_o'}{V_i} = \frac{A_v}{1 - \beta A_v} = A_{vf}$$

$$A_{vf} > A_v$$

used in oscillators where gain is ∞ .

Similarly if feedback is -ve.

$$A_{vf} = \frac{A_v}{1 + \beta A_v}$$

Numericals

V.K Mehta

$$A_{vf} < A_v$$

output < input

* gain is reduced, as well as NOISE &
UNWANTED signal will also
reduce.

Advantages of Negative Feedback :-


- (i) used in operational amplifiers
- (ii) noise & distortion is reduced.
- (iii) performance of device is enhanced.
- (iv) bandwidth of amplifier will also increase.

* Operational Amplifier (Op-Amp).


Op-Amp is a directly coupled multistage voltage amplifier with very high

Op-amps are used to perform various mathematical operat's like add", sub, div, multiplicat" etc.


Block Diagram

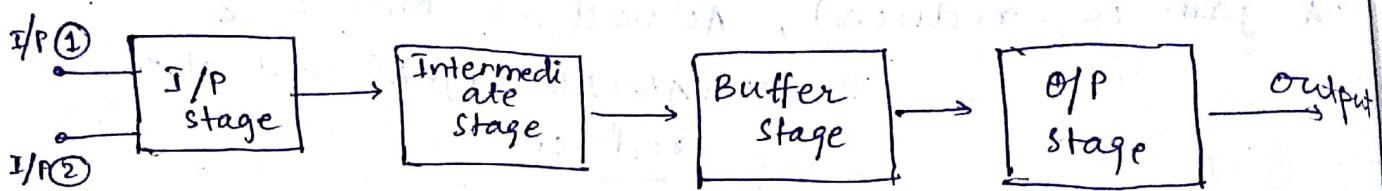

Symbols.

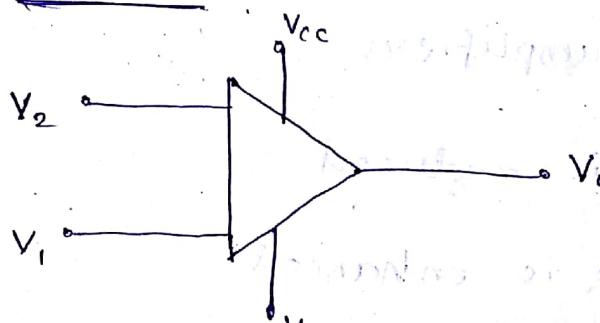


* Open-Loop Differential Gain. Op-Amp.

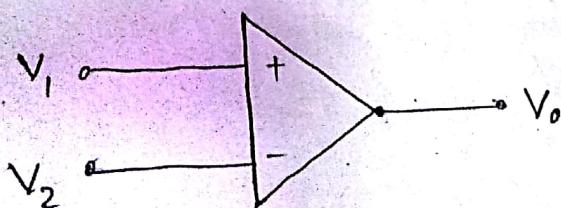

$$\begin{aligned} \text{Gain (A)} &= \frac{\text{Out}}{\text{In}} \\ &= \frac{V_0}{(V_1 - V_2)} \end{aligned}$$

* Study Closed-Loop Diff. Gain Op-amp.

* Non-Inverting Mode Op-Amp :-

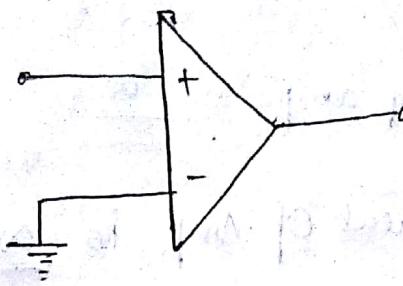


$$A = \frac{V_o}{V_i}$$

$$V_o = AV_i$$

Phase diff. betw' O/P & I/P is ZERO.


* Inverting Mode Op-Amp :-

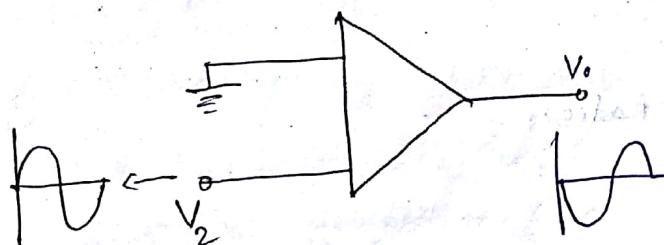

$$V_o = -AV_2$$

'-' denotes out
of phase
by 180° .

VIRTUAL GROUND CONCEPT :

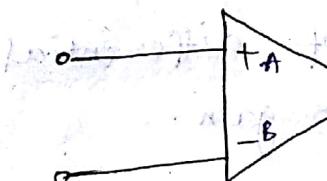

There will be no current flow betw' inv. & non-inv. terminals inside the op-amp because of very high INPUT IMPEDANCE.

* The input impedance of an op-amp is very high which suggests that there is no current flow between inverting & non-inverting terminals inside the op-amp. This is possible only when we consider both of pt A & B are at same potential or grounded virtually. This is called virtual Ground concept.

* Open Parameters / Characteristics.

(i) Infinite Voltage Gain

Gain of ideal op-amp is ∞ . $A \Rightarrow \infty$

(ii) Input Impedance for Ideal Op-Amp is ∞ ($r \rightarrow \infty$)


(iii) Output $n \cdot n \cdot n \cdot n \cdot n = \underline{\underline{O}}(R \rightarrow O)$

(iv) for Ideal Op-Amp,

Band Width = ∞ .

(v) C M R R. (f)

Common Mode Reject" Ratio.

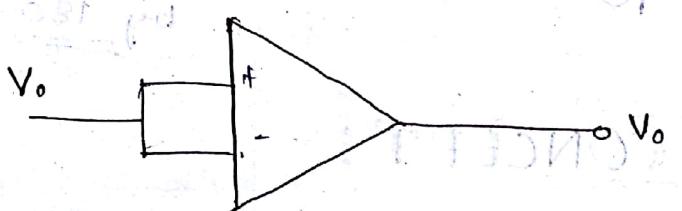

CMRR is defined as the ratio of differential Gain & common mode voltage gain.

$$f = \frac{A_{\text{diff}}}{A_{\text{comm}}}$$

$$(CMRR)_{AB} = 20 \cdot \log_{10} \left(\frac{A_d}{A_c} \right)$$

for ideal op-amp $\rightarrow \underline{\text{CMRR}} \rightarrow \infty$

(vi) SLEW RATE :-

It is defined as the max^m rate of change of output voltage w.r.t time.

(Here the time is measured in μsec.)
micro.sec.

$$SR = \left(\frac{dV_o}{dt} \right)_{\text{max}}$$

unit \rightarrow Volt/sec.

(vii) P.S.R.R. :-

Power Supply Rejection Ratio
PSRR is defined as the input offset voltage due to change in the supply voltage producing it, keeping other power supply voltage constant.

if $V_{EE} \rightarrow \text{const.}$, then

$$PSRR = \left(\frac{\Delta V_{in-off}}{\Delta V_{EE}} \right)$$


if $V_{cc} \rightarrow \text{const.}$, then

$$PSRR = \left(\frac{\Delta V_{in-off}}{\Delta V_{cc}} \right)$$

OFFSET VOLTAGES



* OFFSET RANGE :-

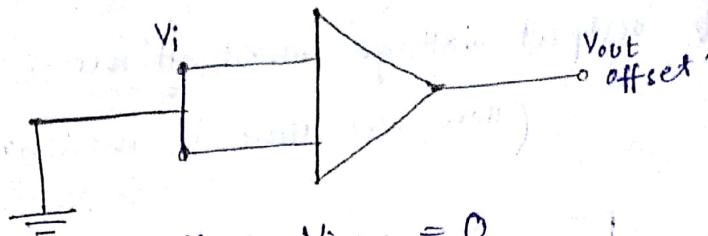

when $V_{input} = 0$

but $V_{out} \neq 0$

then the output voltage is called output offset.


* When both the input terminals are connected to ground $V_{in} = 0$, the output of the op-amp should be ideally 0, but practically, there exists some dc voltage at the output, even the input voltage is zero.

→ This voltage at the output is called Offset Voltage.

To make the output offset voltage zero, a small voltage is to be applied at one of the input terminal.

Such a voltage in input which makes the output offset voltage zero, is called input offset voltage.

* CLOSED LOOP OPAMP GAIN :-

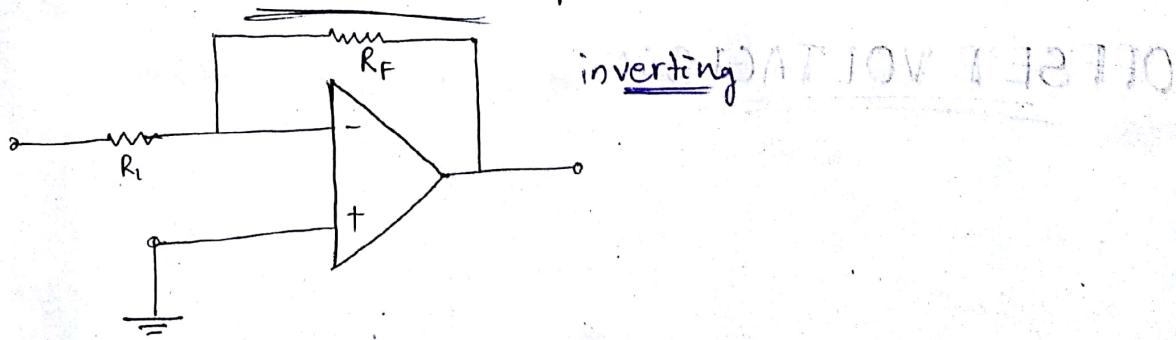

The closed loop op-amp can be designed by feeding some part of output, back to the input using resistance.

* The feedback used in op-amp is always negative.

* The gain resulting with feedback is called closed loop op-amp gain.

* Advantages of Negative Feedback:-

(i) It reduces the gain makes it controllable.


(ii) Negative feedback reduces the distortion.

(iii) increases the bandwidth.

(iv) input resistance of op-amp is increased also.
output resistance is decreased.

* INVERTING

AMPLIFIER:-

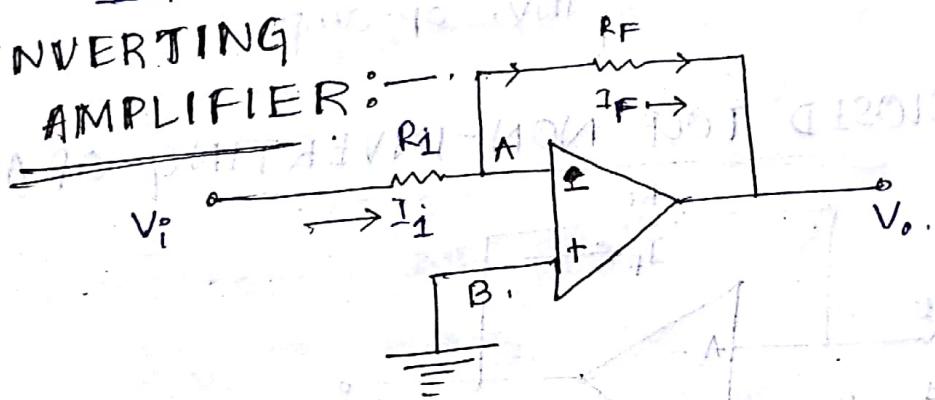

In inverting Amplifier, output voltage is amplified & 180° out of phase wrt input signal.

Due to virtual ground concept :- $V_A = V_B = 0$.

$$I_1 = I_F$$

From Input site,

$$I_1 = -\frac{V_A + V_i}{R_i} = +\frac{V_i}{R_i}$$

from O/P site

$$I_F = \frac{V_A - V_o}{R_F} = -\frac{V_o}{R_F} \quad \text{--- (2)}$$


since

$$I_o = I_F \cdot f \quad (\text{with open loop gain } f)$$

$$\Rightarrow \frac{V_{i_{in}}}{R_{i_{in}}} = \frac{V_o}{R_F} \quad (\text{with feedback}) \quad \text{(3)}$$

$$A_v = \frac{V_o}{V_i} = \frac{-R_F}{R_{i_{in}}} \quad \rightarrow \begin{array}{l} \text{Gain in} \\ \text{closed loop} \\ \text{inv. op-amp} \end{array}$$

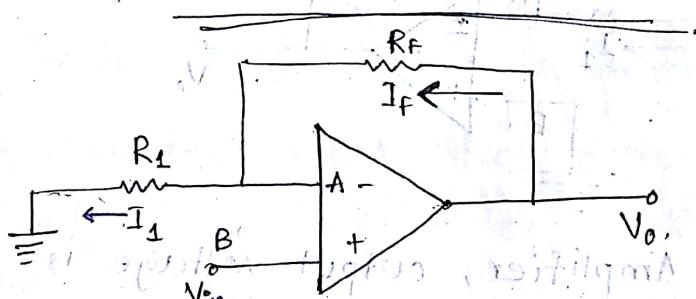* GAIN of CLOSED LOOP NON-INVERTING OP-AMP:



(i) output & input in same phase.

$$(ii) V_A = V_B = V_{in} \quad \rightarrow \text{due to virtual ground concept.}$$

At input side:-

$$I_{i_{in}} = \frac{V_i - 0}{R_1} = \frac{V_i}{R_1} \quad \text{--- (1)}$$

from output side:-

$$I_F = \frac{V_o - V_A}{R_F} = \frac{V_o - V_i}{R_F} \quad \text{--- (2)}$$

Since $I_i = I_f$.


$$\Rightarrow \frac{V_i}{R_i} = \frac{V_o - V_i}{R_F}$$

$$2) R_F V_i = V_o R_i - V_i R_i$$

$$\Rightarrow \frac{V_o}{V_i} = \frac{(R_F + R_i)}{R_i}$$

$$\boxed{\frac{V_o}{V_i} = 1 + \frac{R_F}{R_i}}$$


Q.

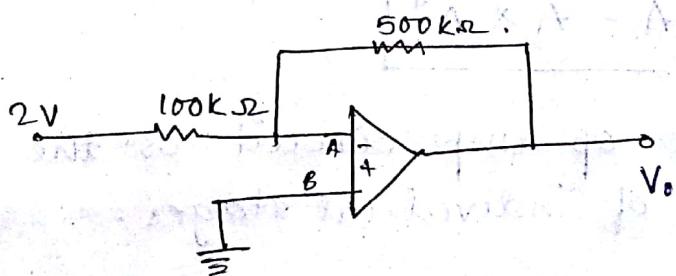


$$\frac{V_o}{2} = -\frac{500}{100}$$

$$\Rightarrow V_o = -10 \text{ V}$$

Q.

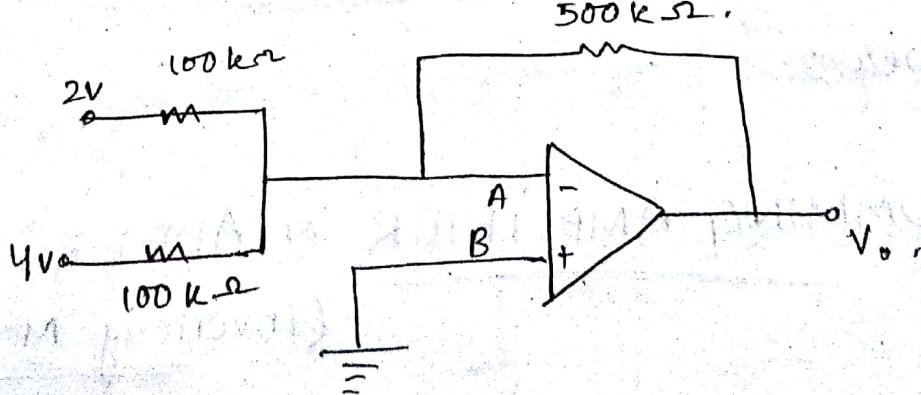

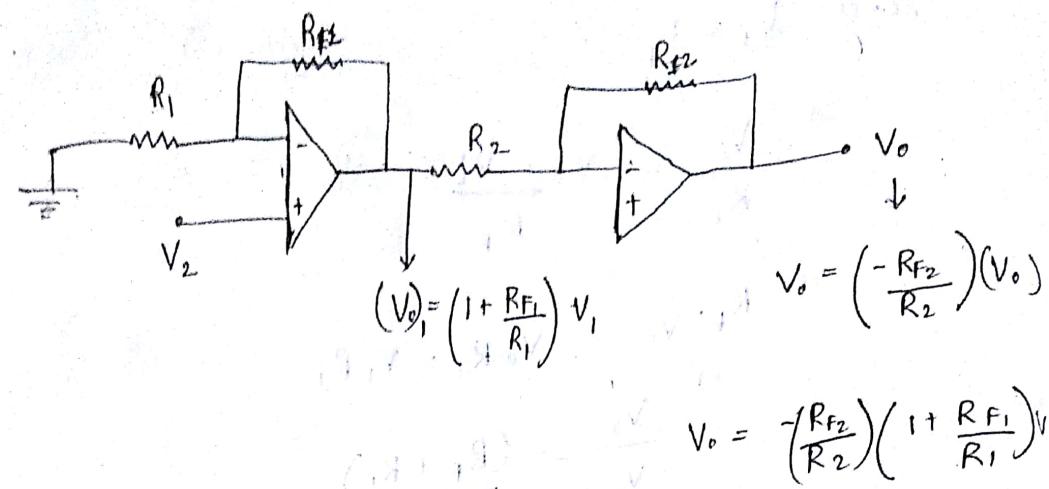


$$\therefore \frac{V_0}{V_2} = A = -\left(\frac{R_{F2}}{R_2}\right) \left(1 + \frac{R_{F1}}{R_1}\right)$$

$$A = A' \times A''$$

Total Gain of Multistage op-amp circuit is the product of the gain of individual stages.

- * Uses Op-Amp
 1. Op-Amp is used as summing Amplifier or Adder.
 2. Integrator
 3. Differentiator
 4. Voltage follower

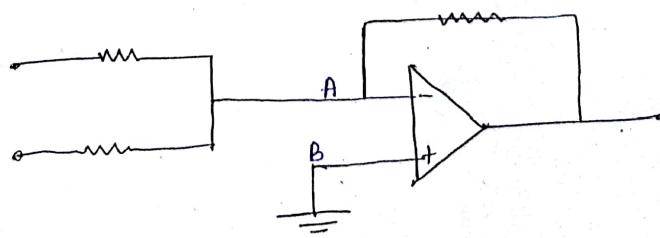→ Op-Amp as SUMMING AMPLIFIER or ADDER (Inverting Mode).



- * In summing Amplifier, o/p voltage is the addition of Input Voltages.
- * From virtual ground concept:-

$$V_B = V_A = 0$$

I/P side \rightarrow

$$I_1 = \frac{V_1 - 0}{R_1} = \frac{V_1}{R_1} \quad \textcircled{1}$$

$$I_2 = \frac{V_2}{R_2} \quad \textcircled{2}$$

$$I_f = \frac{0 - V_o}{R_F} = -\frac{V_o}{R_F} \quad \textcircled{3}$$

$$\therefore I_F = I_1 + I_2$$


$$-\frac{V_o}{R_F} = \frac{V_1}{R_1} + \frac{V_2}{R_2}$$

$$V_o = -\left(\frac{V_1}{R_1} + \frac{V_2}{R_2}\right) R_F$$

if $R_1 = R_2 = R_F$.

$$\Rightarrow V_o = -(V_1 + V_2)$$

* OP-AMP as INTEGRATOR:

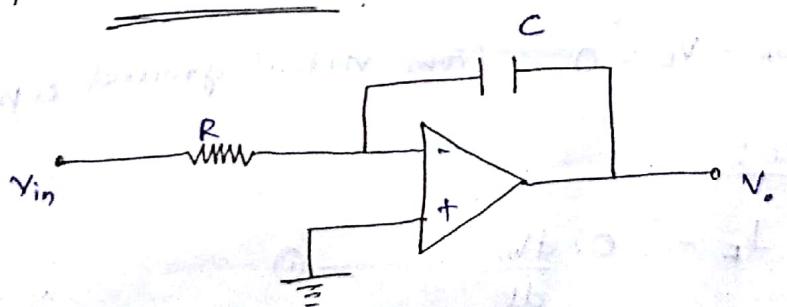

In integrator circuit, o/p is the integralⁿ of I/P voltage.

From virtual ground concept,

$$V_A = V_B = 0$$

I/P

$$I_1 = \frac{V_{in}}{R_1}$$

O/P side

$$I_F = (-C_F) \cdot \frac{dV_o}{dt}$$


$$I_F = I_1$$

$$\frac{dV_o}{dt} = \frac{V_m}{R_1}$$

$$\frac{dV_o}{dt} = -\frac{1}{R_1 C_F} (V_{in} \cdot dt)$$

$$\Rightarrow V_o = -\frac{1}{R_1 C_F} \int V_m \cdot dt$$

* OP-Amp as DIFFERENTIATOR :-

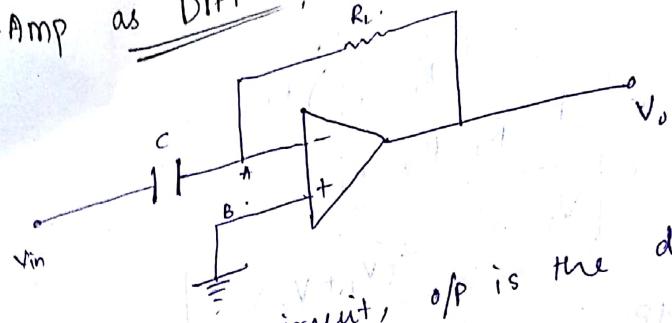

In differentiating circuit, o/p is the differential of I/P waveform from virtual ground concept

$$V_A = V_B = 0$$

I/P side :

$$I_F = C \cdot \frac{dV_m}{dt} \quad \text{--- (1)}$$




O/P side

$$I_R = \frac{V_A - V_o}{R_F} = -\frac{V_o}{R_F} \quad \text{--- (2)}$$

$$\therefore I_R = I_F$$

$$-\frac{V_o}{R_F} = C \cdot \frac{dV_m}{dt}$$
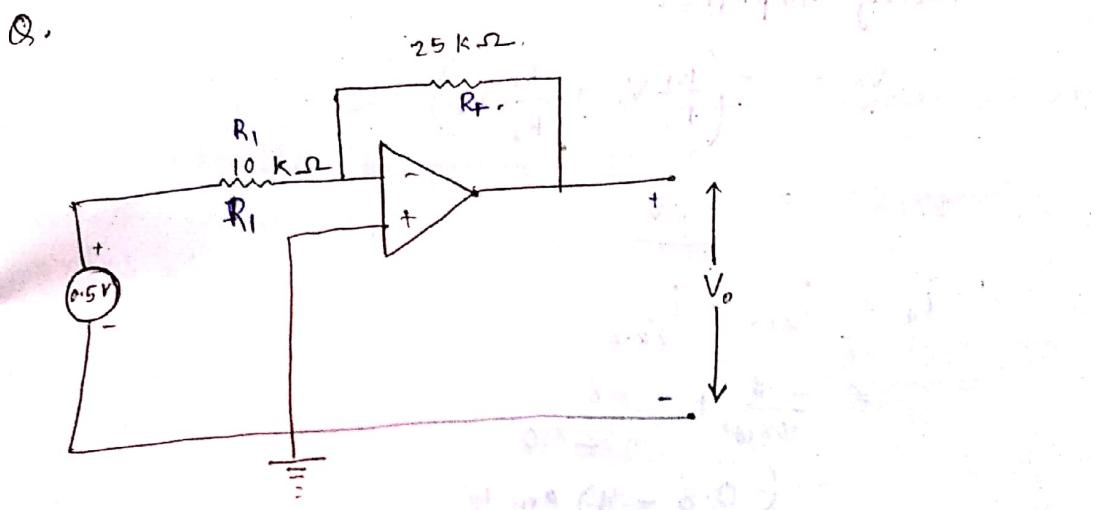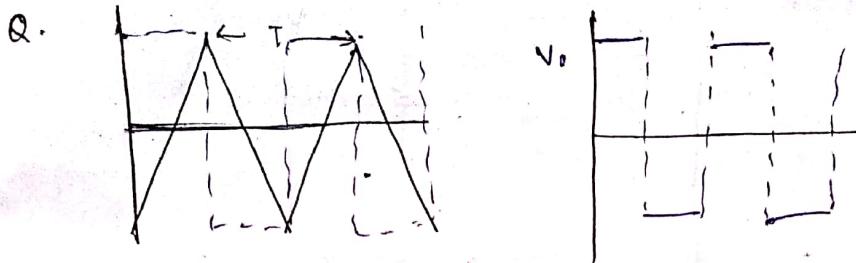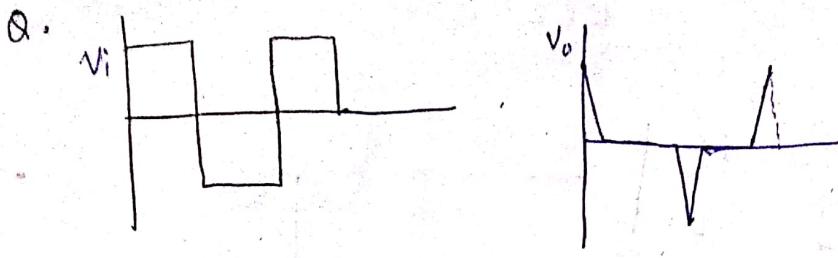
$$\Rightarrow V_o = -R_F C \frac{dV_m}{dt}$$




$$\frac{V_o}{V_{in}} = -\frac{R_F}{R_1} = -\frac{25}{10}$$


$$\Rightarrow V_o = -\frac{25}{10} \times 0.5 = -1.25$$

$$i_1 = \frac{(0.5 - 0)}{10 \times 10^3} = 0.5 \times 10^{-4}$$

~~for 0.05 mA~~

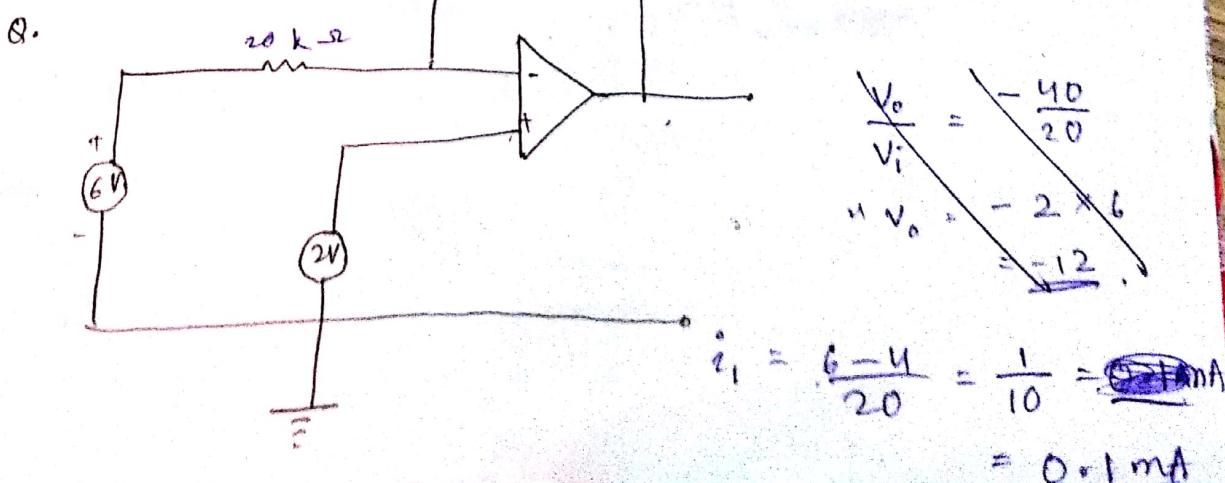

Q.

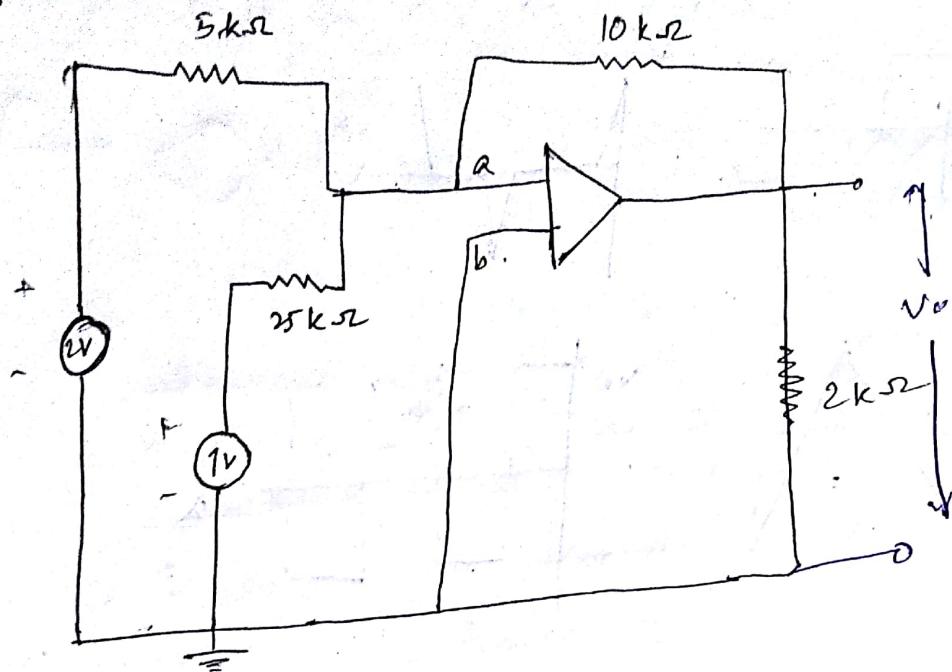

summing Amplifier

$$V_o = - \left(\frac{R_F}{R_1} V_1 + \frac{R_F}{R_2} V_2 \right)$$
$$= - \underline{\underline{8V}}$$

$$i_o = i_{in, 10k\Omega} + i_{in, 2k\Omega}$$
$$= \frac{-8}{10 \times 10^3} + \frac{-8}{2 \times 10^3}$$
$$= (-0.8 - 4) \text{ mA}$$
$$= \underline{\underline{-4.8 \text{ mA}}}$$